

Digital & Mixed Signal Design (EE559)

Project

Name: Anish Madurai Narayanamurthy

Person# 50249279

Name: Aritra Manna


Person# 50245595

Objective

Our objective is to design a fast-settling, fully differential switched-capacitor amplifier with a gain of 2. The design aim is to be able to meet the specifications while minimizing power and maximizing settling speed.

Introduction

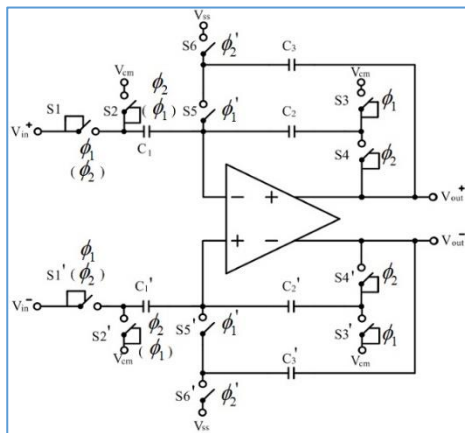Analog signal amplification in discrete-time system can be performed by switched-capacitor amplifiers. Switched-capacitor amplifier has been used in the design of digital-to-analog converter. Below is the circuit diagram of a fully differential CMOS switched-capacitor amplifier based on transmission gates logic based switches.



For Miller compensation capacitor circuit

$\frac{g_{m2}}{C_L} > \frac{\sqrt{3}g_{m1}}{C_c}$; Value of $C_c > 0.22 * 1 \text{ pf} = 0.22 \text{ pf}$; we have chosen $C_c = 500 \text{ fF}$; $g_{m2} = 7.25 * 10^{-3} \Omega^{-1}$

Design methodology

Calculations

For single stage opamp

For DC voltage gain = 116.5 dB

$$GBW = g_m * \left(\frac{1}{2\pi C_L} \right) = 200 \text{ MHz (Assuming)}$$

$$g_m = 1.256 * 10^{-3} \Omega^{-1}$$

Now, by using the (g_m/I_d) technique, the transistor sizes of single stage op-amp are (All transistors in saturation):

Transistor	Length	Width
N7,N8	970nm	31.3μm
P5,P4	850nm	113μm

$$\frac{g_m}{I_d} = 13.3444 \text{ V}^{-1}$$

$$\frac{g_m}{I_d} = \frac{1.256 * 10^{-3}}{13.3444}; I_d = 9.412 * 10^{-5} \text{ A}$$

From the above equation $I_{d2} = 5.433 * 10^{-4} \text{ A}$


Transistor Sizing

Transistor	Length	Width
N16,N6	970nm	590μm
P9,P3	850nm	134μm



Sizing of the remaining transistors of the two stage opamp

Transistor	Length	Width
N5	970nm	62.6 μ m
P8,P7	850nm	56.6 μ m
N9	850nm	31.3 μ m
N11	970nm	15.65 μ m
N12,N10	970nm	7.83 μ m

Single stage op-amp

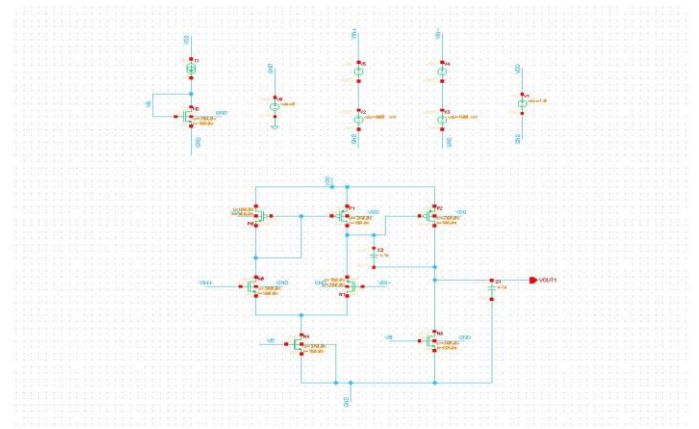


Two-stage fully differential OTA

 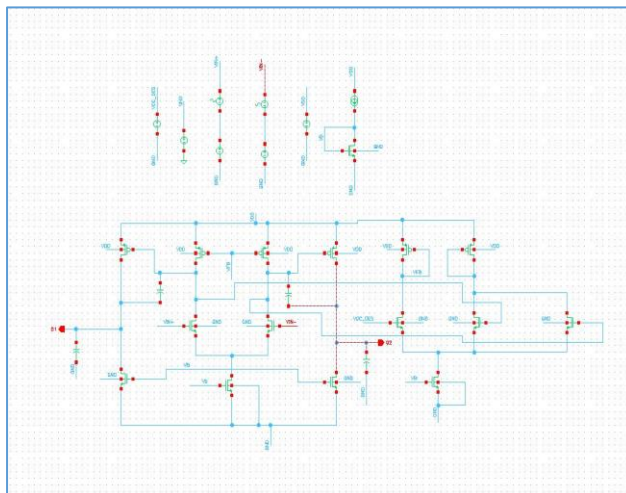


Amplified output 1

Non-overlapping clock generator

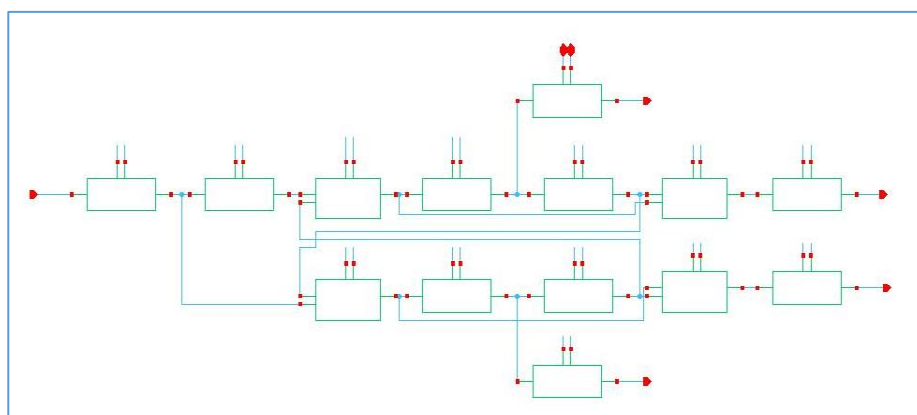



Gain and phase margin

 

Gain: 63.2046 dB

Phase Margin: 63°

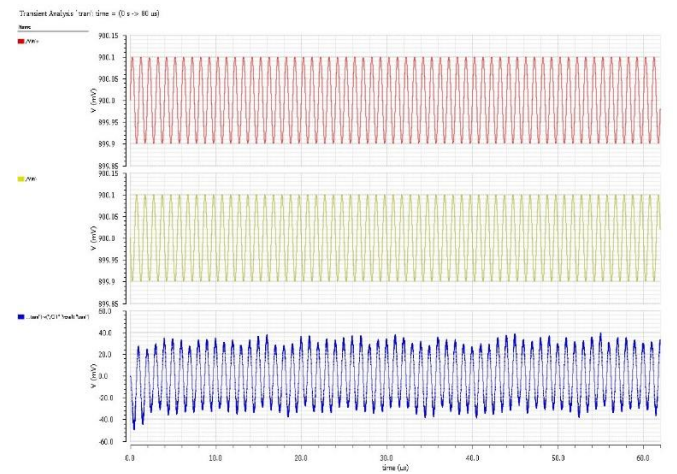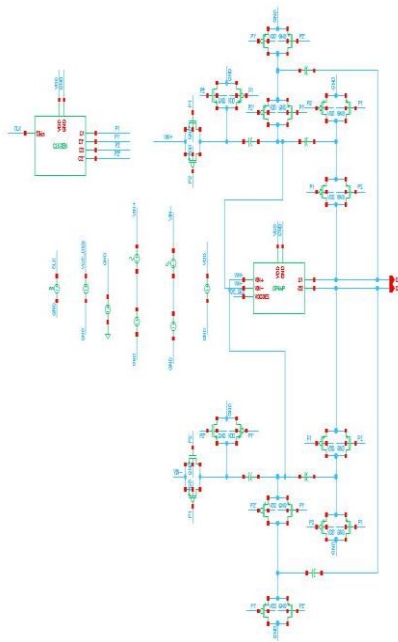Differential switched capacitor amplifier




Amplified output 2

All sizes and passive values of the differential switched capacitor circuit

Transmission gates transistor sizes for the sampling switches	For Pmos(W/L): 20um/5um	For Nmos(W/L): 20um/5um
C_L		10pF
f_s		33kHz
f_{in}		2.5kHz
T_s		30μs
Pulse width		15μs
V_{in}		30μV

The **gain** of the switched capacitor amplifier was found to be above **2** on giving the above values.

 DFT plot of the differential output of the differential switched capacitor circuit



Final calculations:

The SNDR was found out to be **57.043 dB** from the above DFT plot

Power consumption $P=VI$; $1.8V \cdot 80.55\mu A$; $P = 145 \mu W$


The Energy Efficiency number = $57.043 + 10\log(33 \cdot 10^3 / 145 \mu W)$

Energy Efficiency number = 140.61

Static settling error = $\epsilon_s = -1/T$ (where $T = A_v\beta$) where 1336688 is A_v (Voltage ratio) and β is $1/2$; $T = 1.49 \cdot 10^{-6}$ (converting it to db and calculating for settling error)

$\epsilon_s = -118 \text{ db}$

Transient Noise Analysis

 

References

1. A Differential Switched-Capacitor Amplifier KEN MARTIN, MEMBER,IEEE,LEVENT OZCOLAK, MEMBER, IEEE, Y, S, LEE, AND GABOR C. TEMES, FELLOW,IEEE (IEEEJOURNAL OF SOLID-STATECIRCUITS,VOL. SC-22,NO. 1, FEBRUARY1987)
2. FULLY DIFFERENTIAL SWITCHED CAPACITOR AMPLIFIER MODELLING AND PARAMETER EVALUATION Andrei DANCHIV* , Mircea BODEA# , Claudius DANȘ
3. Digital CMOS design by Razavi